HSCD LAB Assignment No. 1

Name : Ashutosh Rajendra Karve

Mail : 2024ht01021@wilp.bits-pilani.ac.in

Contact : +91 9765541324

Date : 18/08/2024


Place : Pune, Maharashtra

Multiplexer Design

What is multiplexer?


Multiplexer is a combinational logic circuit used to select only one input among several inputs based on selection lines.

Task 1: Design 2-to-1 Multiplexer

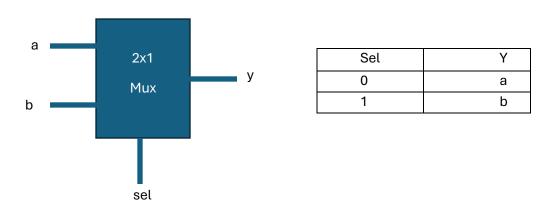


sel	а	b	У
0	0	Х	0
0	1	Х	1
1	Х	0	0
1	Х	1	1


DEFINE MODULE >>

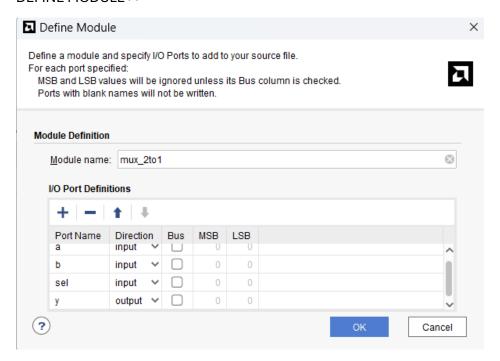


Design Source file >>

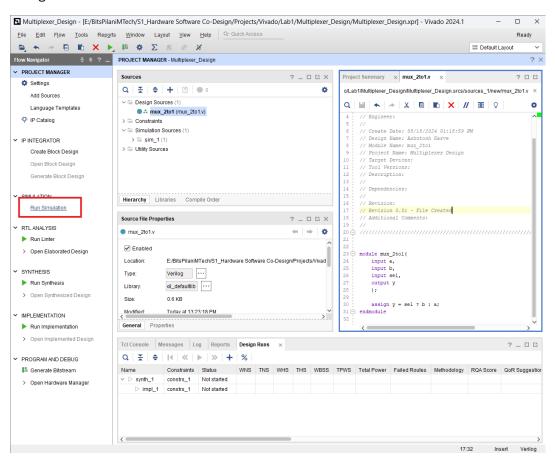


SIMULATION RESULTS 1 >>

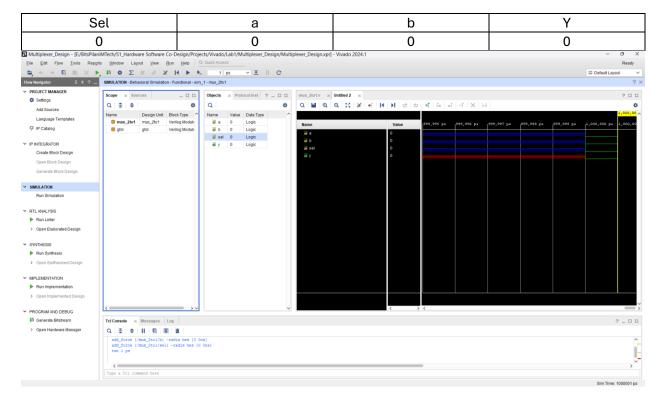


SIMULATION RESULTS 2 >>

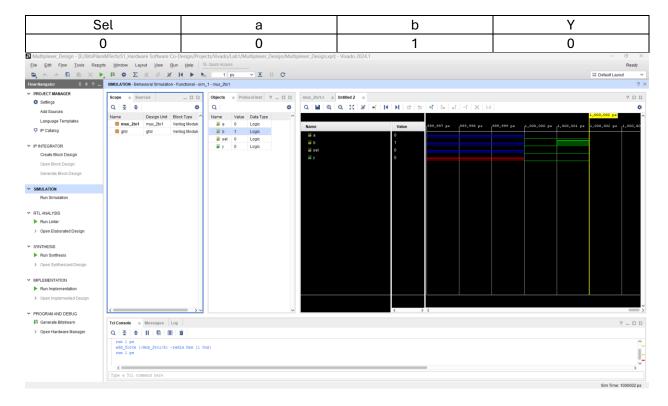


SIMULATION RESULTS 3 >>

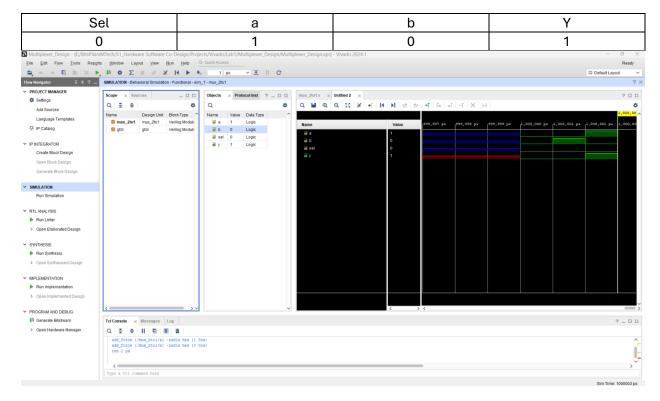


SIMULATION RESULTS 4 >>

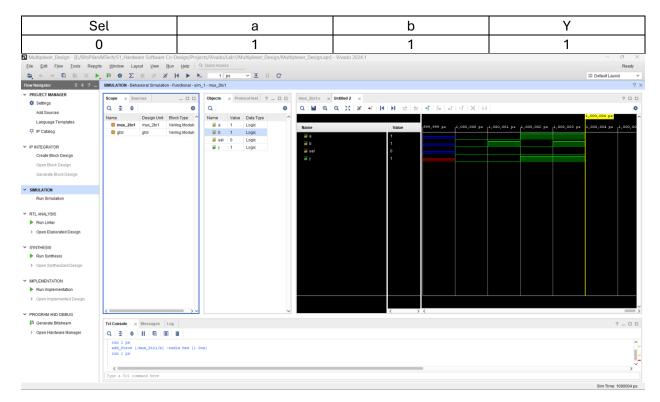


SIMULATION RESULTS 5 >>

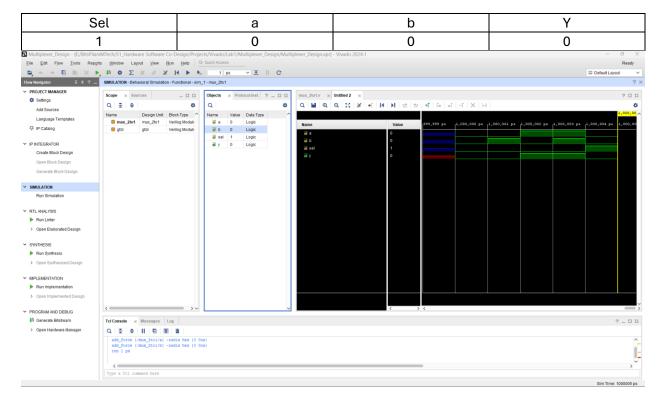


SIMULATION RESULTS 6 >>

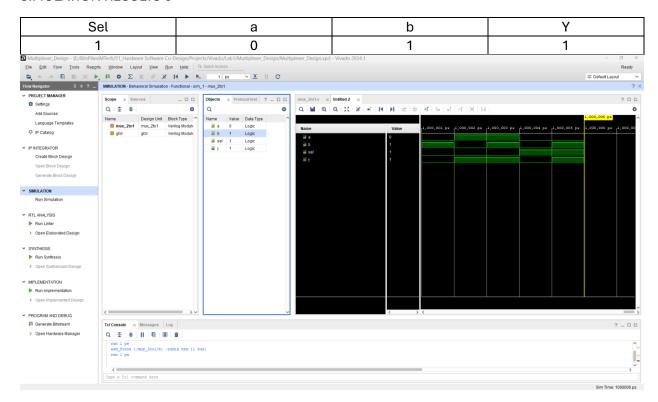


SIMULATION RESULTS 7 >>

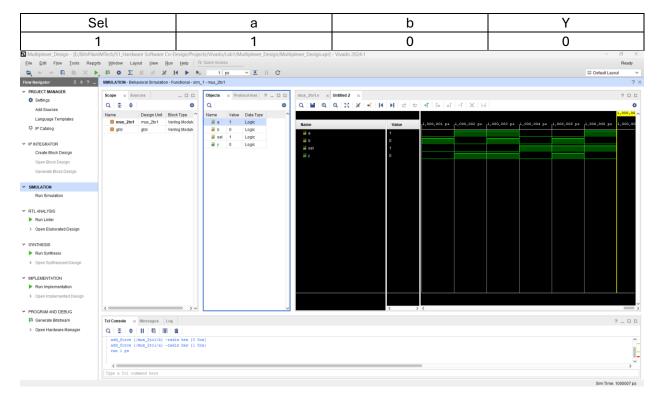


SIMULATION RESULTS 8 >>

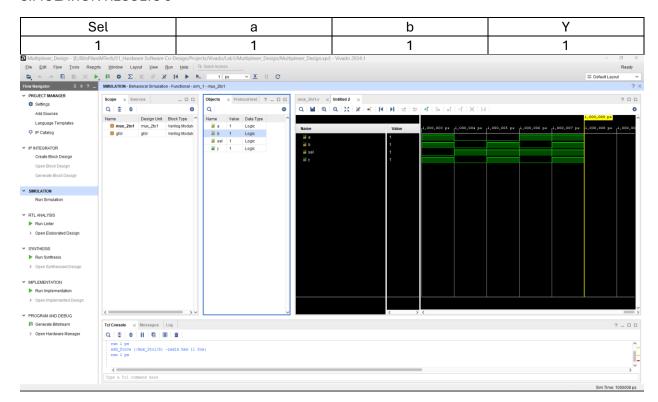


ELABORATED DESIGN >>

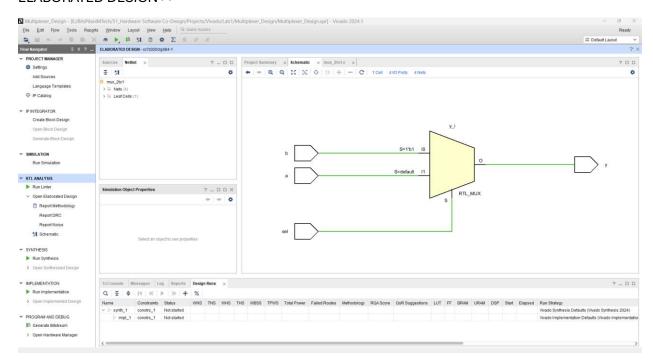

SYNTHESIZED DESIGN >>

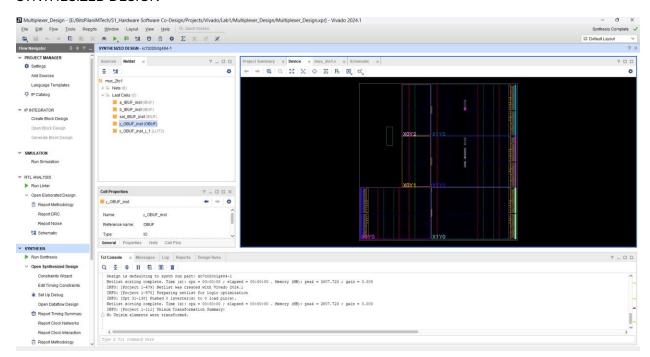


Task 2: Design 4-to-1 Multiplexer

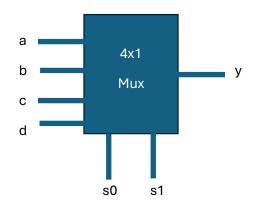


Truth Table

s1	s0	У
0	0	а
0	1	b
1	0	С
1	1	d

DESIGN SOURCE CODE >>

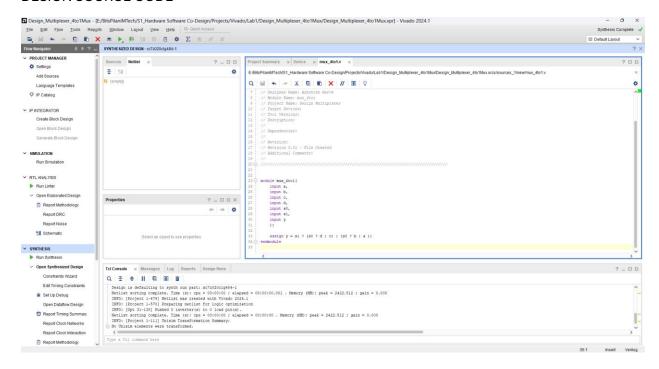

SIMULATION RESULTS 1 >>

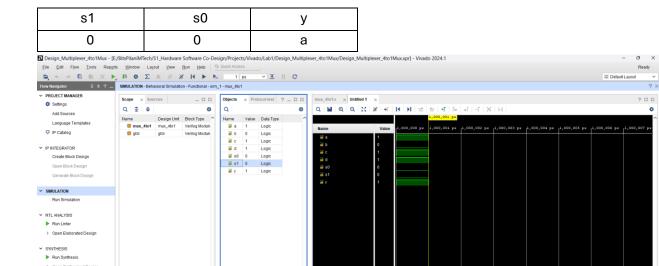

SIMULATION RESULTS 2 >>


➤ IMPLEMENTATION

➤ Run Implementation


➤ Open Implemented Design

➤ PROGRAM AND DEBUG


III Generate Bitstream

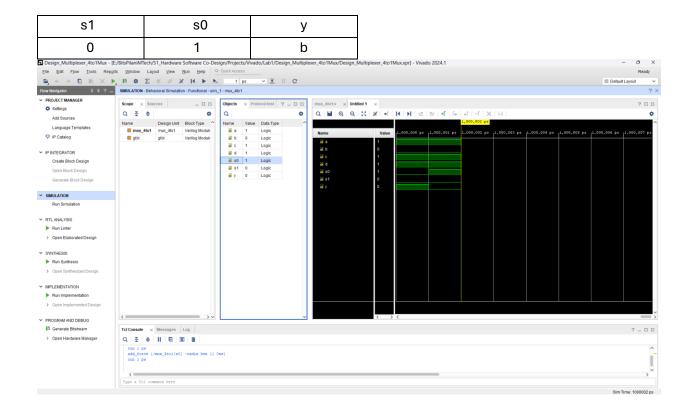


SIMULATION RESULTS 3 >>

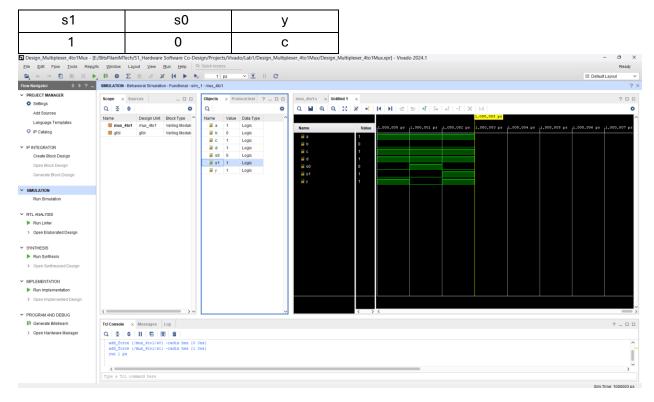


SIMULATION RESULTS 4 >>

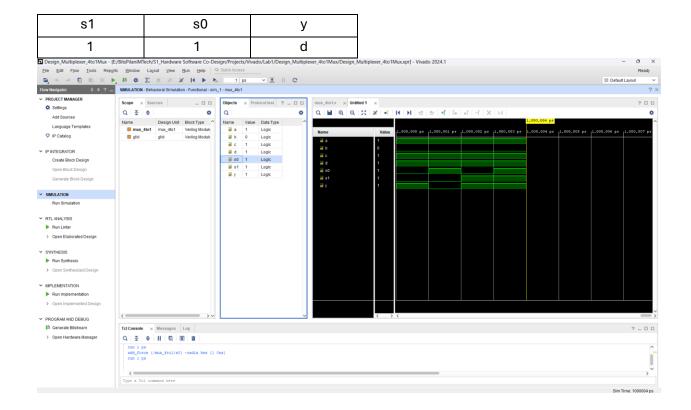

ELABORATION DESIGN >>

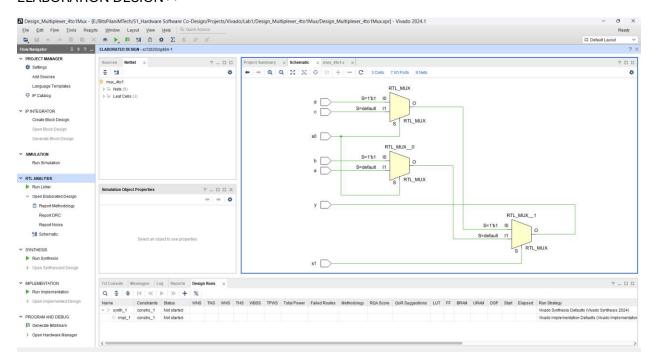


SYNTHESIZED DESIGN >>

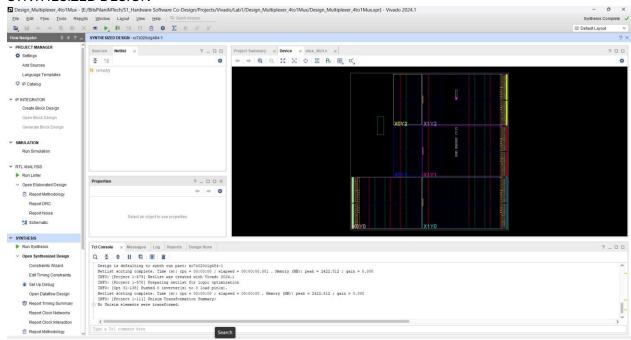


<< BASIC HOW TO CREATE PROJECT IN VIVADO >>

Creating New Project on vivado FPGA >>


Files >> New Proejct

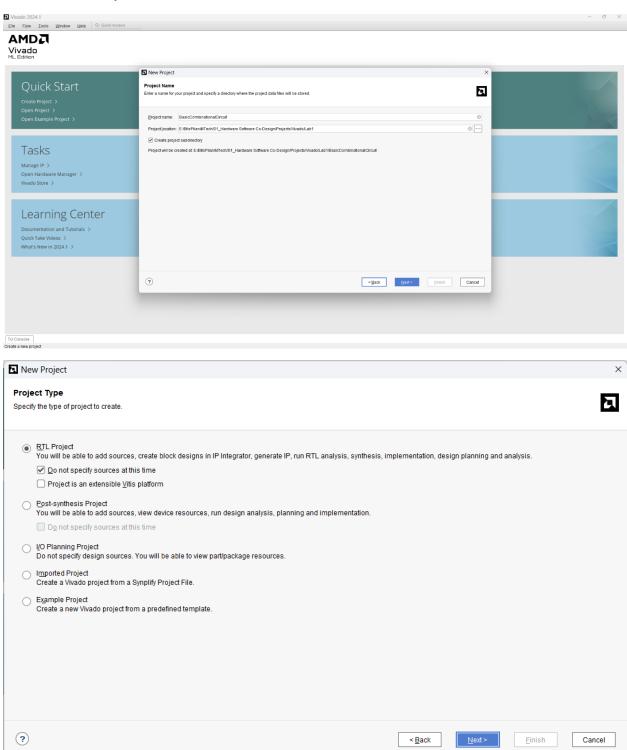


Search for ZedBoard >>

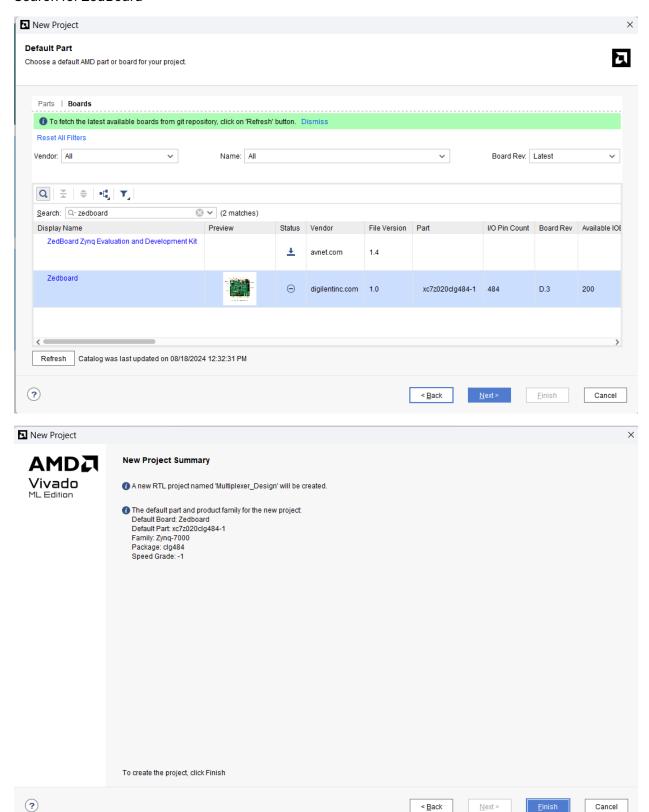


Right Click on >> Design Sources

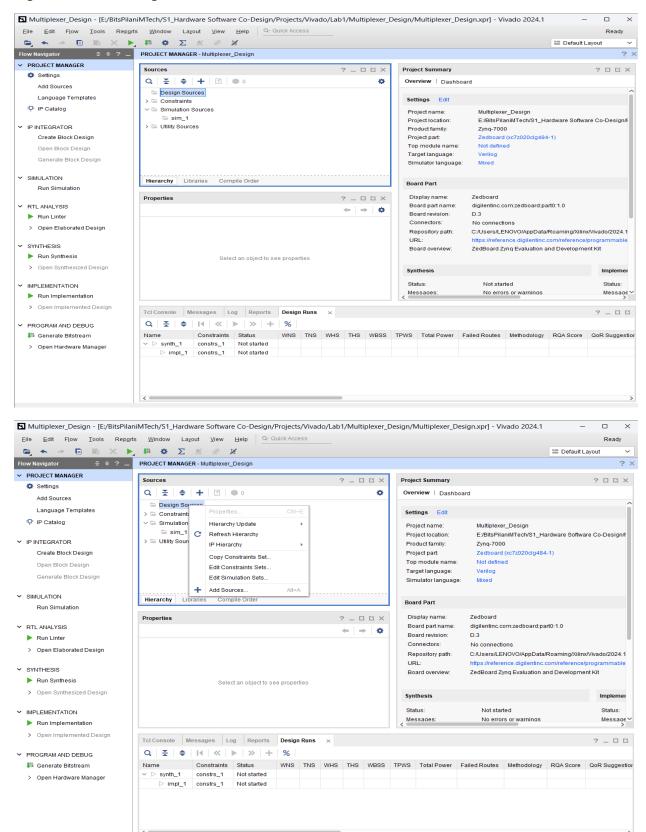

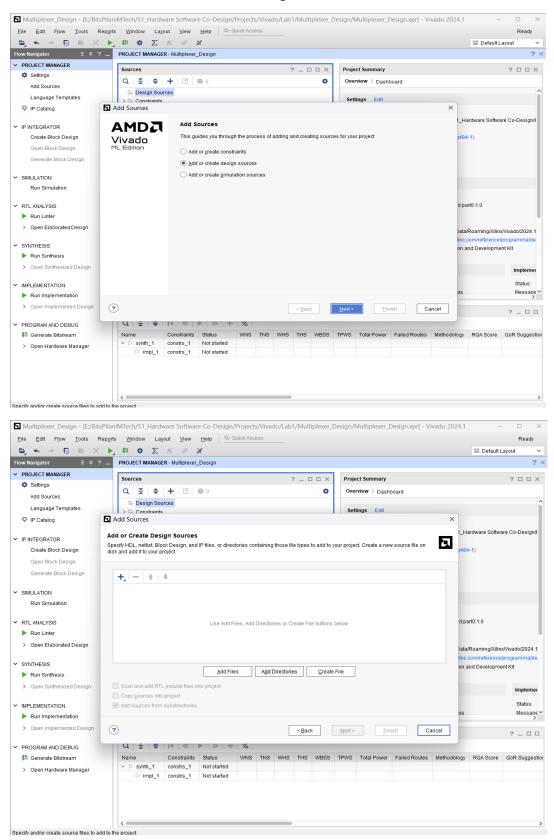Select + Add Sources >> Add or create design sources >> Next



Click >> create File >> File name >> OK

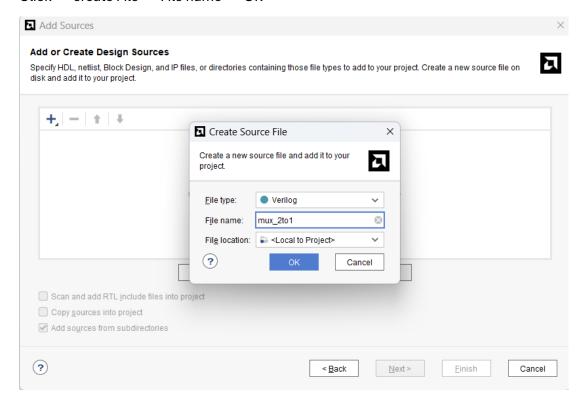

Click >> Finish

